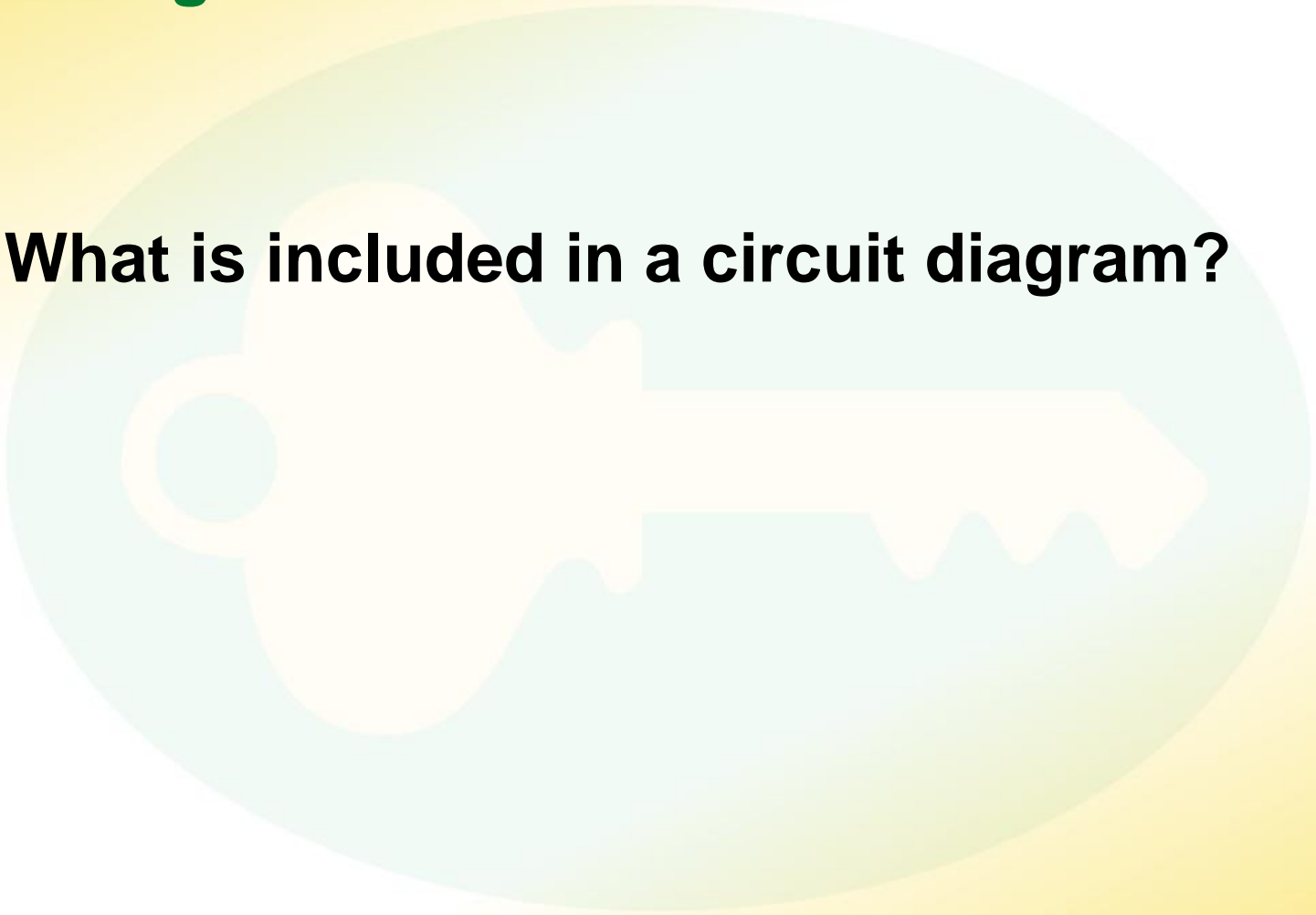


# Circuit Diagrams



**What is included in a circuit diagram?**



## Circuit Diagrams


An **electric circuit** is –

A circuit diagram shows –

## Series Circuits



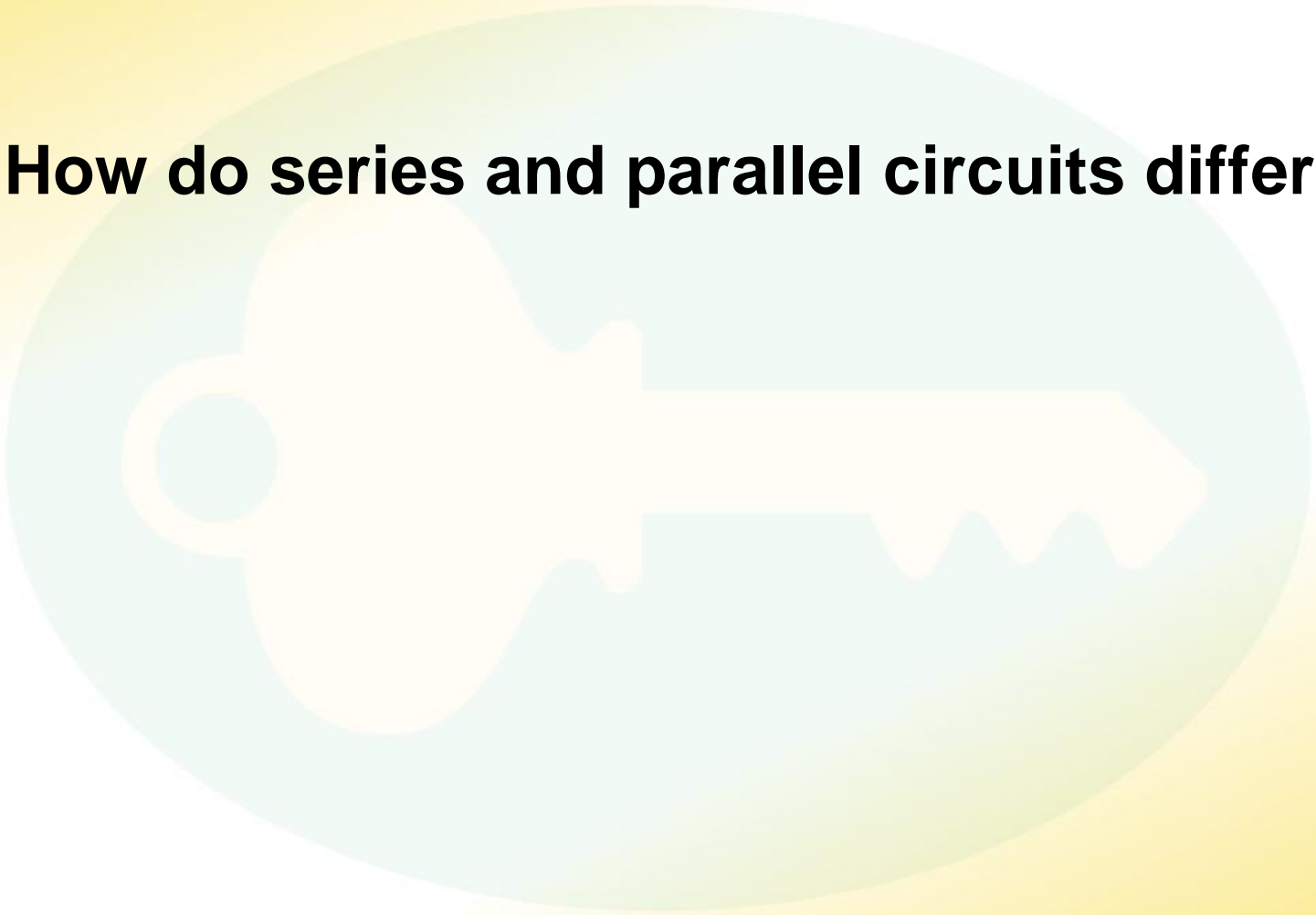**How do series and parallel circuits differ?**



## Series Circuits


In a **series circuit** –

If one bulb burns out in a series circuit –

## 20.3 Electric Circuits

# Series Circuits

A series circuit has –

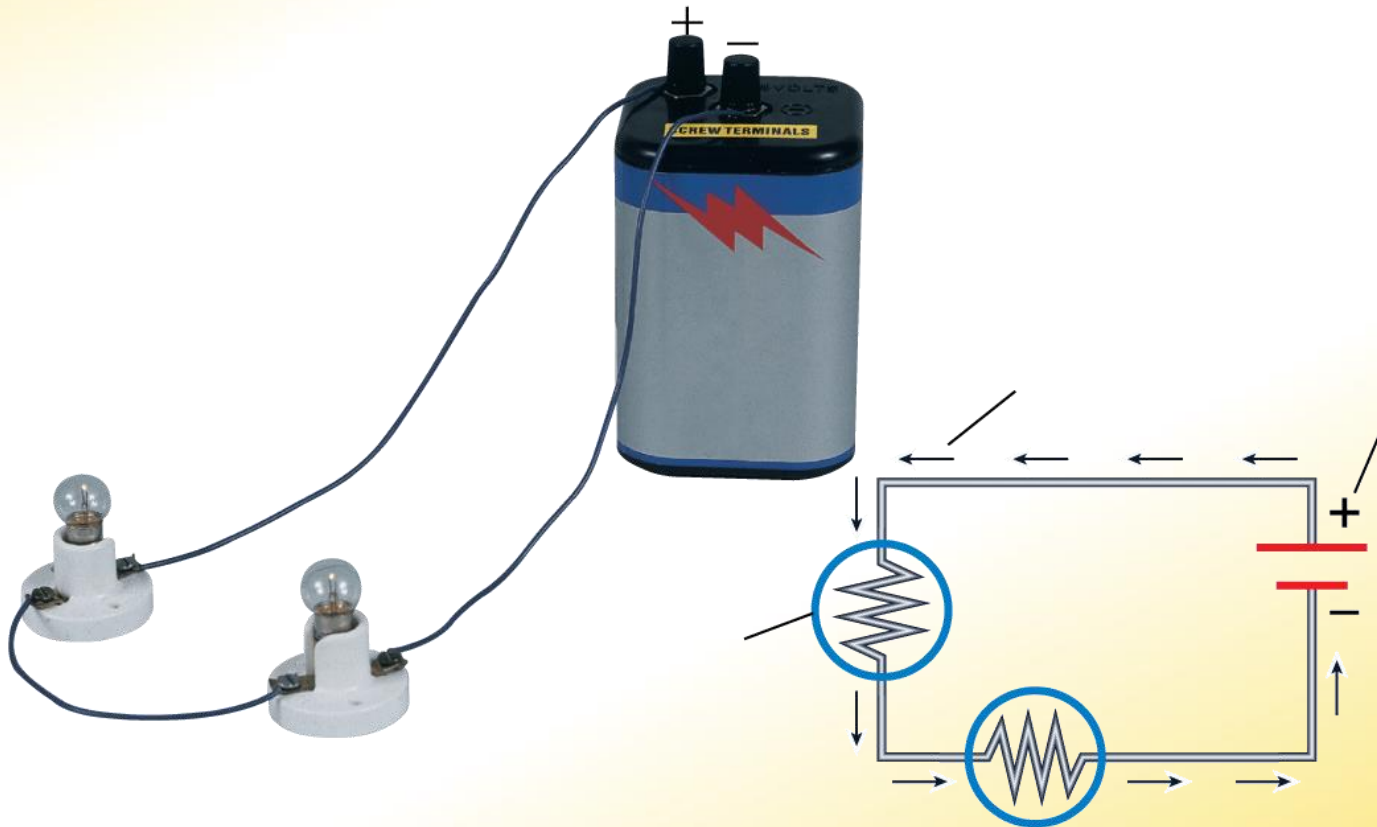


## Parallel Circuits

A **parallel circuit** is –

If one bulb in a parallel circuit burns out –

# Parallel Circuits

A parallel circuit –

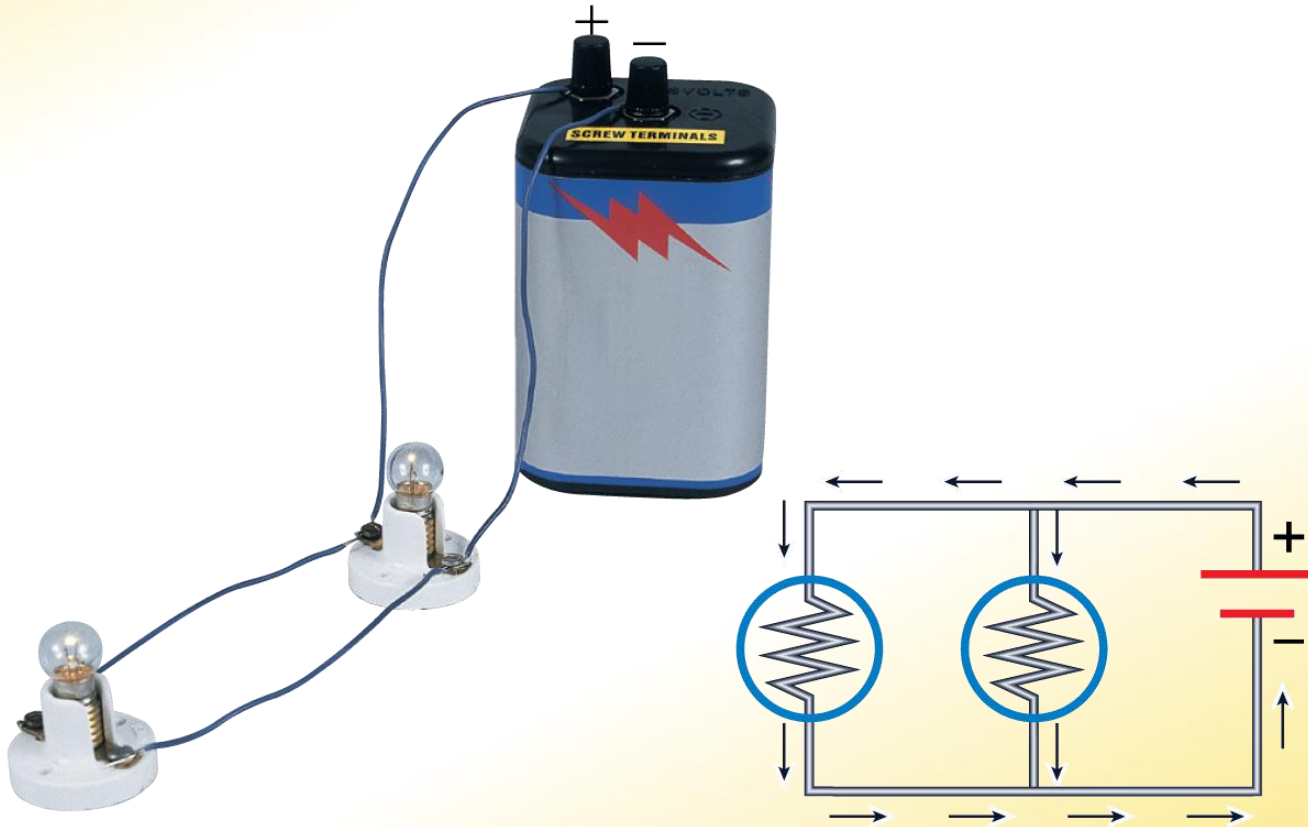

## Power and Energy Calculations



**How do you calculate electric power and electrical energy use?**



## Power and Energy Calculations

**Electric power is –**

The unit of electric power is –

$$P = ?$$

## Power and Energy Calculations

Math Practice

1. A clothes dryer uses about 27 amps of current from a 240-volt line. How much power does it use?

Answer:

## Power and Energy Calculations

Math Practice

2. A camcorder has a power rating of 2.3 watts. If the output voltage from its battery is 7.2 volts, what current does it use?

Answer:

## Power and Energy Calculations

Math Practice

3. A power tool uses about 12 amps of current and has a power rating of 1440 watts. What voltage does the tool require?

Answer:

# Power and Energy Calculations

## Electrical Energy

$$E = P \times t$$

# Electrical Safety



**What devices make electricity safe to use?**



## Electrical Safety

### Home Safety

A fuse –

A circuit breaker is –

# Electrical Safety

## Grounding –



## Electrical Safety

A ground-fault circuit interrupter (GFCI) is –

# Electrical Safety

Even a small current –



Ground-fault circuit interrupter (GFCI)



## Effect of Current on Human Body

Current Level	Effect
1 mA	Slight tingling sensation
5 mA	Slight shock
6–30 mA	Painful shock; loss of muscular control
50–150 mA	Extreme pain; severe muscular contractions. Breathing stops; death is possible.
1000–4300 mA	Nerve damage; heart stops, death is likely.
10,000 mA	Severe burns; heart stops, death is probable.

## Assessment Questions

1. A number of light bulbs are connected to an energy source in a series circuit. What will happen to the other bulbs if one of the bulbs burns out?
  - a. Nothing will happen.
  - b. They will be brighter.
  - c. They will be dimmer.
  - d. They will turn off.

## Assessment Questions

2. A pair of 15-watt computer speakers are connected to a 12-volt power supply. What is the electric current running through the speakers?
- a. 0.8 A
  - b. 1.25 A
  - c. 12.5 A
  - d. 180 A

## Assessment Questions

1. A ground-fault circuit interrupter is a switch that opens to prevent overheating when the current in a circuit is too high.

True

False